

Name of the Student: G. Manasa	Academic Year: 2024-28
Student Registration Number: 241U1R3007	Year & Term: II&I
Study Level: UG	Class & Section: CSE-DS
Name of the Course: Digital Electronics	Name of the Instructor: Nuzhath Farhana
Name of the Assessment: Lab Report-3	Date of Submission: 03-08-2025

Lab Report 3

Simulation of Boolean Expressions using Logic Gates


Objective: To implement and verify the functionality of Boolean expressions using basic logic gates in SimulIDE.

Software Used: SimulIDE

Circuit Diagrams:

Boolean Algebra Examples No1



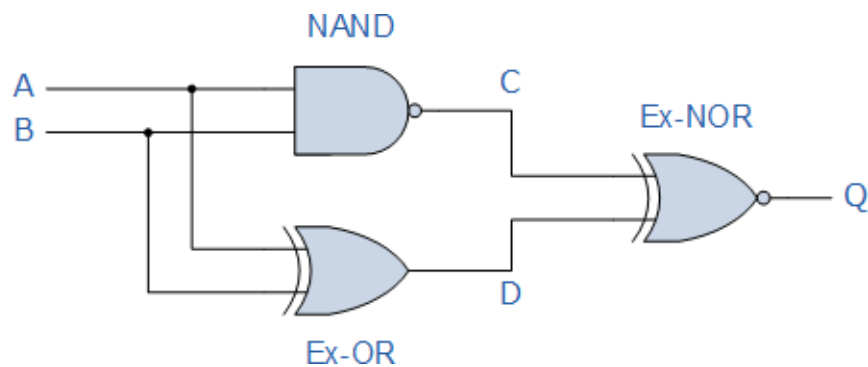
Construct a Truth Table for the logical functions at points C, D and Q in the following circuit and




identify a single logic gate that can be used to replace the whole circuit.

Inputs		Output at		
A	B	C	D	Q
0	0	1	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	0	1

Circuit Executions

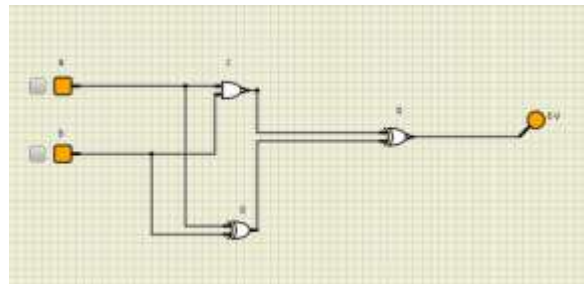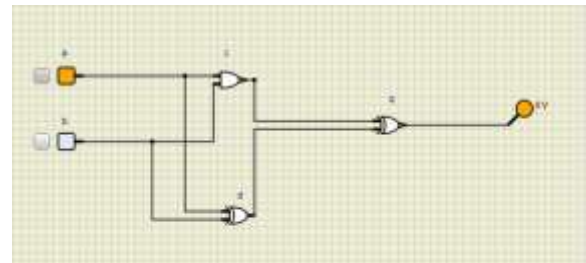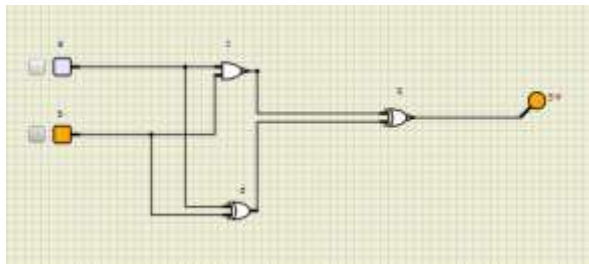





Boolean Algebra Examples

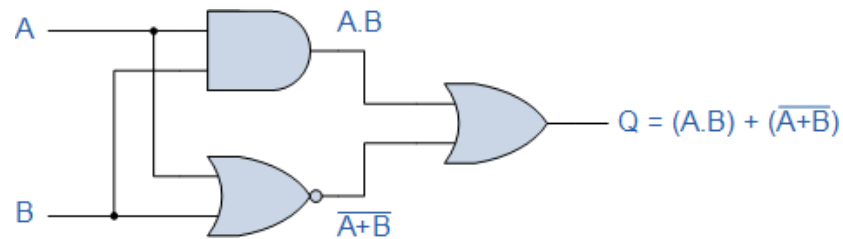

The output of the system is given as $Q = (A.B) + (A+B)'$ but the notation $A'+B'$ is the same as the De Morgan's notation $A'.B'$. Then substituting $A'.B'$ into the output expression gives us a final output notation of $Q = (A.B) + (A'.B')$, which is the Boolean notation for an Exclusive- NOR Gate

Inputs		Intermediates		Output
B	A	$A.B$	$\overline{A+B}$	Q
0	0	0	1	1
0	1	0	0	0
1	0	0	0	0
1	1	1	0	1

Circuit Executions:

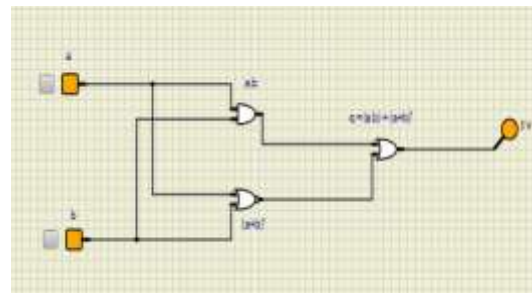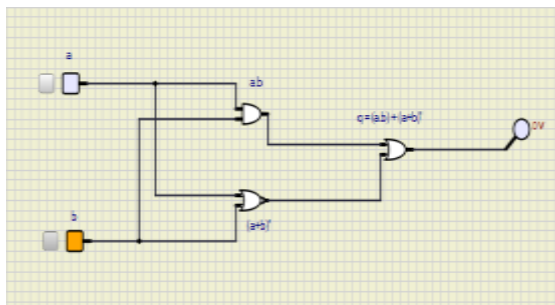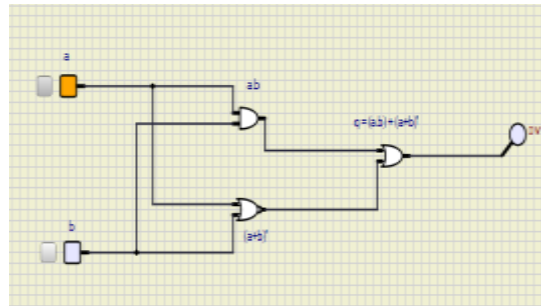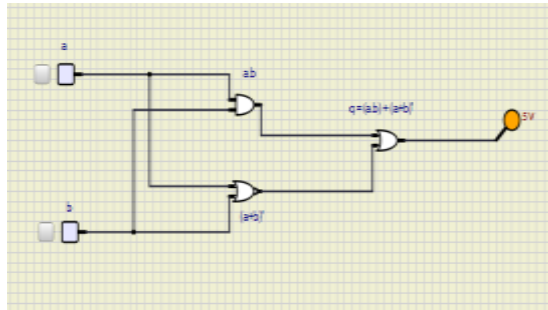


DeMorgan's Theorem

DeMorgan's Theorem and Laws can be used to find the equivalency of the NAND and NOR gates

DeMorgan's First Theorem

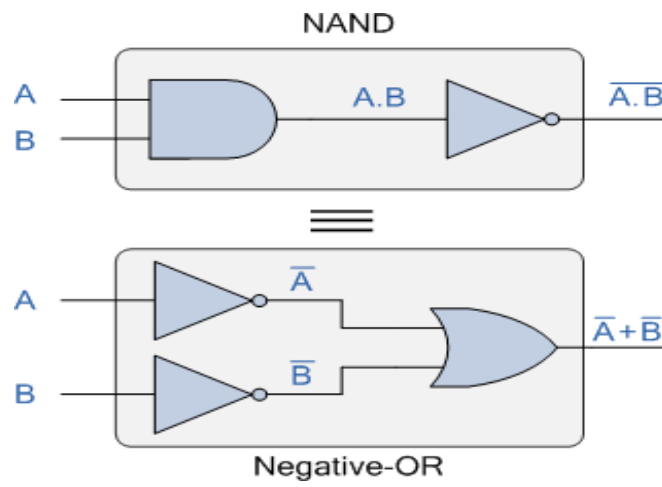DeMorgan's First theorem proves that when two (or more) input variables are AND'ed and negated, they are equivalent to the OR of the complements of the individual variables. Thus the equivalent of the NAND function will be a negative-OR function, proving that $A.B = A+B$. We can show this operation using the following table.




Verifying DeMorgan's First Theorem using Truth Table

Inputs		Truth Table Outputs for Each Term				
B	A	A . B	$\overline{A . B}$	A	B	$\overline{A + B}$
0	0	0	1	1	1	1
0	1	0	1	0	1	1
1	0	0	1	1	0	1
1	1	1	0	0	0	0



We can also show that $A.B = \overline{A+B}$ using logic gates as shown.

Circuit Executions:

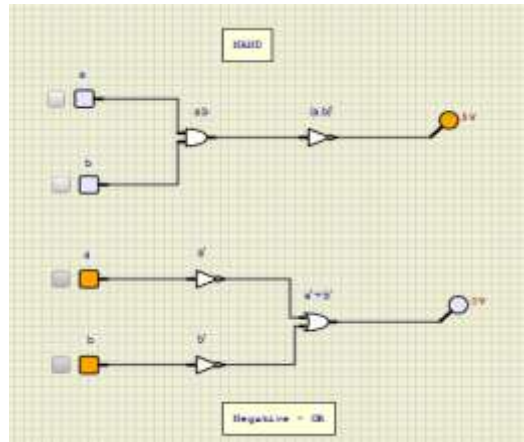

We can also show that $A.B = A+B$ using logic gates as shown.


Circuit Executions:

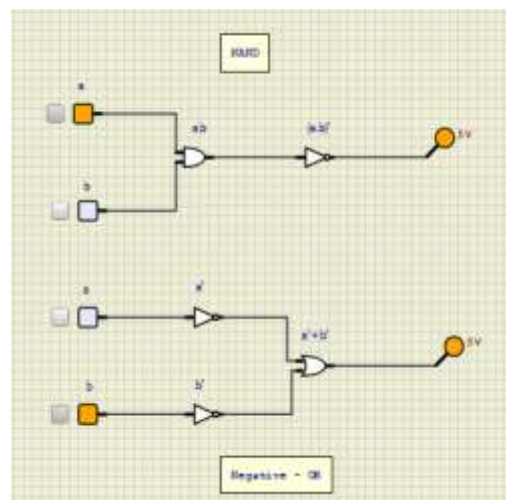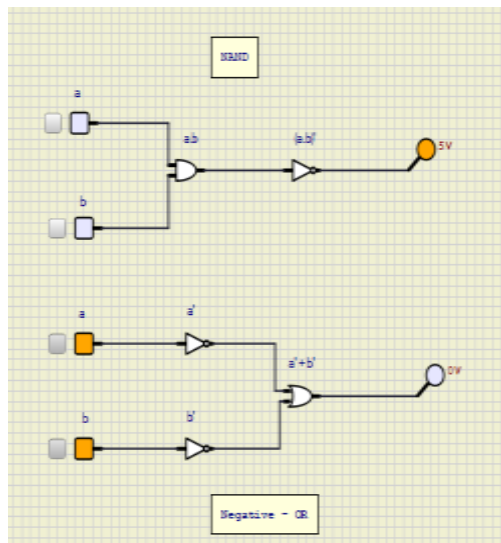

DeMorgan's Second Theorem

DeMorgan's Second theorem proves that when two (or more) input variables are OR'ed and negated, they are equivalent to the AND of the complements of the individual variables. Thus the equivalent of the NOR function is a negative-AND function proving that $A+B = A.B$, and again we can show operation this using the following truth table.


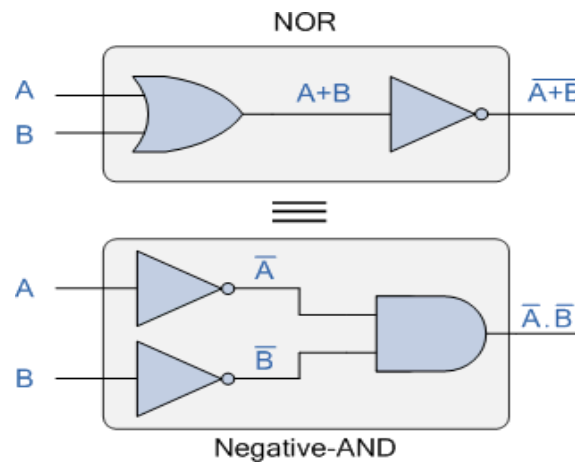
DeMorgan's Second Law Implementation using Logic Gates





Verifying DeMorgan's Second Theorem using Truth Table

Inputs		Truth Table Outputs for Each Term				
B	A	A+B	$\overline{A+B}$	$\overline{A}$	$\overline{B}$	$\overline{A} \cdot \overline{B}$
0	0	0	1	1	1	1
0	1	1	0	0	1	0
1	0	1	0	1	0	0
1	1	1	0	0	0	0

Circuit Executions:

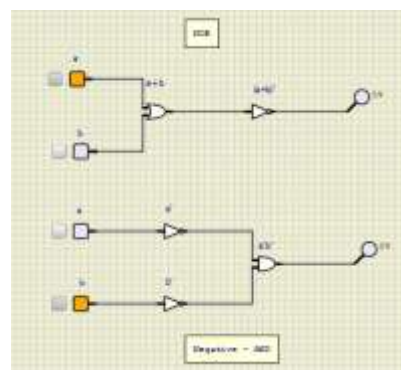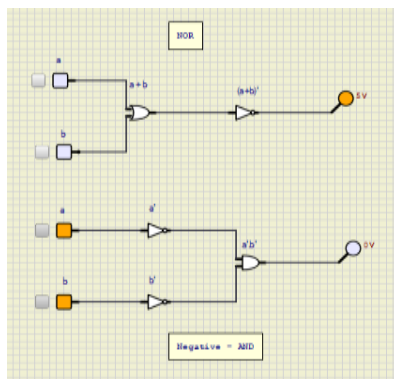

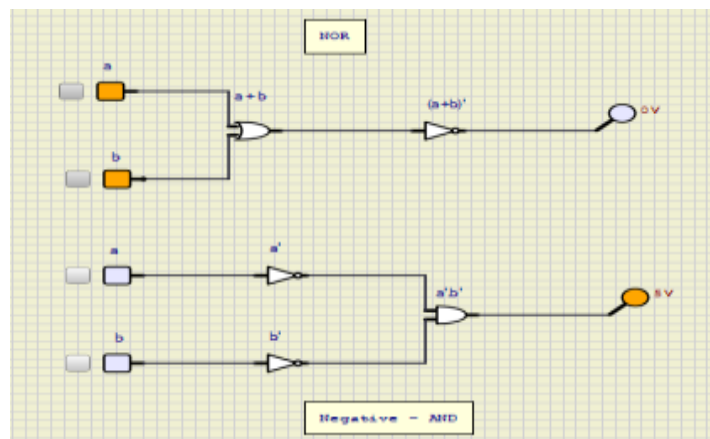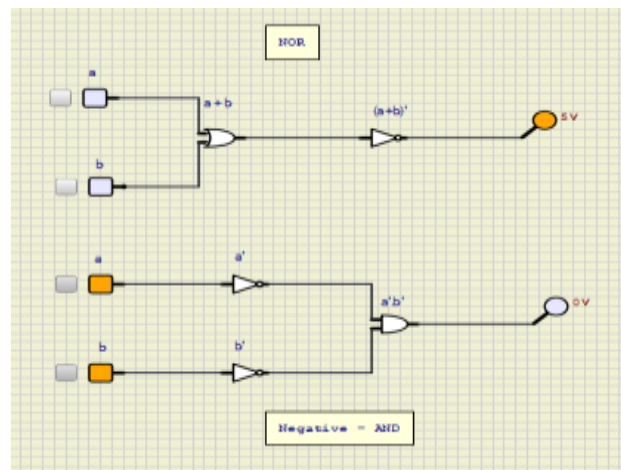

Results:

- Boolean expressions were successfully implemented in SimulIDE.
- Output matched expected values in the truth table.
- Circuit diagrams were verified and tested for various input combination.